


Development of FPCCD Readout ASIC

'08 3/5 Y. Takubo
(Tohoku university)

Introduction


FPCCD vertex detector

 - Pixel size : $5\mu\text{m}$
- Thickness : $15\mu\text{m}$
- Signal level : $\sim 500e$ for large angle
- Readout channel : 16 or 32 ch
 - $\sim 20,000 \times 128$ pix/ch




Test-sample will be delivered in 2008.

 - Pixel size : $12\mu\text{m}$
- Readout channel : 4ch
 - 512×128 pix/ch




Layout of FPCCD test-sample

 

Motivation to develop readout ASIC

Motivation to develop readout ASIC

 - The FPCCD test-sample will be delivered in the end of this year.
- The FPCCD has a large number of readout pixels.
 - Test sample : 512 x 128 pix/ch
- There is no readout ASIC suitable for the FPCCD.



Readout ASIC for the FPCCD is necessary.

- For FPCCD test-sample
- To establish readout technique

Requirement to the readout ASIC

Requirement to the readout ASIC



- All elements to operate and read FPCCD are contained in one chip.
- **Readout rate : >10 Mpix/sec**
 - $[20000 \times 128 \text{ pix}]/[0.2 \text{ s}]$
- **Noise level of the ASIC : < 30 electrons**
 - Required total noise level including the CCD : <50 electrons
 - Noise level of FPCCD : ~ 30 electrons
- **Power consumption : < 6 mW/ch**
 - The power consumption in a cryostat should be <100 W.
 - Required total power consumption : <16 mW/ch ($\sim 100\text{W}/6000\text{ch}$)
 - CCD : $\sim 10\text{mW}/\text{ch}$

To achieve these requirement, readout ASIC is designed.

Design concept of readout ASIC

ASIC elements

  - Voltage amplifier
- LPF (Low-pass filter)
- CDS (Correlated double sampling)
- ADC
 - 2 charge sharing ADC are used alternatively to achieve 10Mpix/sec.
- LVDS driver




The design was optimized with SPICE simulation.


Design optimization with SPICE

- The SPICE simulation was applied to design the readout ASIC.
- The design was optimized for 0.35 μm process by TSMC.

Logic design of the readout ASIC

 

Logic design of the readout channels

 


Each elements were checked with simulation.

Expected performance

Expected performance

- Readout rate : 10 Mpix/sec **→ OK!**
 - Data conversion rate : 10MHz (= 5x2 MHz)
 - 260 ms/ch : [20000 x 128 pix/ch] x [10⁻⁷ s/pix]
- Power consumption < 5 mW/ch **→ OK!**
 - Charge-sharing ADC realizes low power. (~10 μW)
- Noise level : ~10e **→ OK!**
 - Estimation with SPICE simulation.

 The performance will satisfy our requirement.




The prototype of the readout ASIC was produced.

Readout ASIC


Readout ASIC prototype

- The layout was made by Digian technology.
- The chip was produced by MOSIS.
 - Size : 2.85 x 2.85 mm²
 - # of pad : 80
 - Readout channel : 8
- The chip was covered by QFP-80pin package.

ASIC layout

 

Readout ASIC with package

 


Test-bench was constructed to perform the response test.


Block diagram of test-bench

VME-based system was developed for the test-bench.

 - Operation and data acquisition is done by VME-GPIO module.
- Response of the readout ASIC was checked, connecting to GPIO.



Test bench


 


Response test

Test menu

- Monitor output
 - After gain-amplifier
 - Differential signal before ADC
- Gain adjustment
- ADC output

The response test was performed.

  


Analog monitor output


Monitor output was checked at the timing of test-pulse.

- All monitor output can be observed.

 → **The amplifier, LPF, and CDS are working.**



 Response of adjustment block for gain was checked.




Gain adjustment


The monitor output was checked, changing the amplifier gain.

- Adjustment of the gain is done by the operation signal from outside.
- The pulse height could be changed by the setting the gain.

 → The adjustment block for the amplifier gain is working!



Gain : x 2

 


ADC output

The output from ADC was checked.

- Serial output from ADC was confirmed.

 → All components in the readout ASIC is working!



The next step is to investigate the performance.

Summary

- The readout ASIC for FPCCD was developed.
- Response test of the readout ASIC was started.
- The output of analog monitor was checked.
 - The amplifier, LPF, CDS are working.
 - The amplifier gain can be adjusted by the operation signal from outside.
- The serial output from ADC was confirmed.
- All components in the readout ASIC are working.
- The next step is performance study.